

EELE 250: Circuits, Devices, and Motors

Balanced three-phase circuits

Assignment Reminder

- Read 5.7 AND 15.1 - 15.2
- Exam #3: Wednesday, November 9, in class. The coverage will be amplifier concepts and operational amplifier circuit analysis.
- No lab, quiz, or practice problems this week.
- Lab #7 formal report due next week.
- Veterans Day holiday on Friday: no MSU classes; offices closed.

Electrical Power Distribution

- In the United States and most of the world, electrical power is distributed as sinusoidal alternating voltage and current (AC), with three separate conductors and *phases*.
- The three sinusoidal phases are spaced by 120°

$$v_a(t) = V \cos(\omega t)$$

$$v_b(t) = V \cos(\omega t - 120^\circ)$$

$$v_c(t) = V \cos(\omega t + 120^\circ)$$


$$\mathbf{V}_a = V \angle 0$$

$$\mathbf{V}_b = V \angle -120$$


$$\mathbf{V}_c = V \angle 120$$

Three-phase source


“Wye”
configuration
with neutral

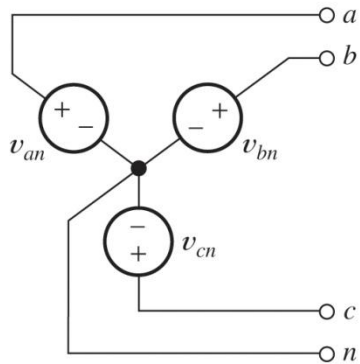

(a) Three-phase source

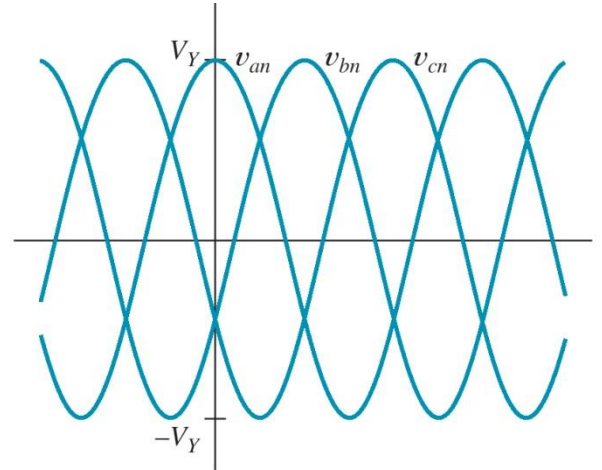


(b) Voltages versus time

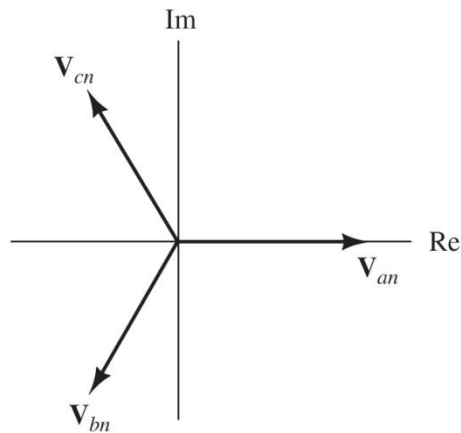

(c) Phasor diagram

Three-phase wye-wye connection

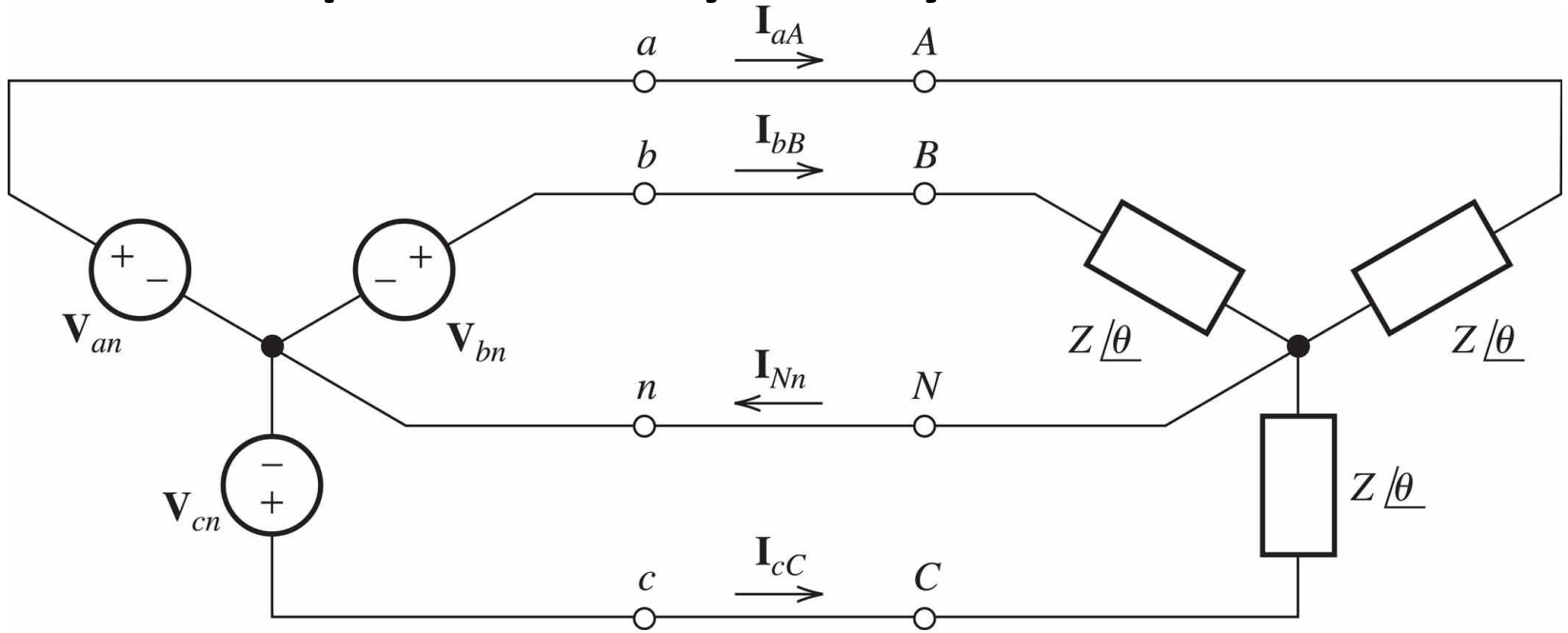

$$I_{aA} = \frac{V_{an}}{Z \angle \theta} = \frac{V_Y \angle 0^\circ}{Z \angle \theta} = I_L \angle -\theta$$

$$\begin{aligned} I_{Nn} &= I_{aA} + I_{bB} + I_{cC} \\ &= \left[I_L \angle -\theta \right] + \left[I_L \angle -120^\circ - \theta \right] + \left[I_L \angle 120^\circ - \theta \right] \\ &= 0 \end{aligned}$$

Three-phase power

- With a single phase, the power fluctuates with time: $\cos^2(\omega t)$
- With three-phase connection, the power delivered by each phase is offset in time such that the total power is constant with time
- Three-phase motors receive constant power, and can therefore deliver constant torque
- Also, fewer conductors are needed to deliver three balanced phases compared to three separate phases.